



Amplifiers with Negative and Positive Feedback

Team 2: Energon

Presented to -

Mr. Md. Atikul Islam

Lecturer, Department of Computer Science and Engineering

Daffodil International University

Our Team


- 01 Sanzida Akter Nupur
ID: 232-15-759
- 02 Md Shahinur Kabir Antor
ID: 232-15-159
- 03 Supan Roy
ID: 232-15-716
- 04 Pallab Debnath
ID: 232-15-676

- 05 Umme Arifa Zaman Nirjhor
ID: 232-15-695
- 06 Foysal Mahamud Fahim
ID: 232-15-334
- 07 Sharmin Akter Jame
ID: 232-15-380





Presenter 1

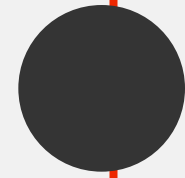

Sanzida Akter Nupur
ID: 232-15-759

Area Covered

1. Introduction to Amplifiers and Feedback
2. Negative Feedback Basics, Principle and Gain
3. Positive Feedback Basics and Gain of Voltage
4. Mathematical Problems
5. Advantages of Negative Feedback in Amplifiers
6. Comparison between Positive and Negative Feedback
7. Conclusion


Introduction to Amplifiers and Feedback

What is an Amplifier?

- A device that boosts weak input signals to a higher output level.
- Widely used in audio systems, communication devices, and signal processing.

Feedback in Amplifiers

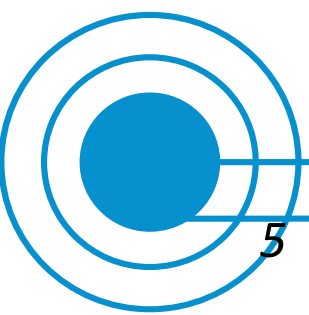- Feedback occurs when a portion of the output is returned to the input.
- Purpose: Helps control and improve amplifier performance.



Introduction to Amplifiers and Feedback

Types of Feedback

Negative Feedback:

- Reduces the overall gain of the amplifier.
- Increases stability, reduces distortion, and widens bandwidth.

Positive Feedback:


- Increases the amplifier's gain.
- Can lead to oscillations, useful for creating oscillators in circuits.

Importance of Feedback

- Essential in designing stable and efficient amplifier circuits.
- Choice of feedback type impacts the amplifier's functionality and application.



Presenter 2

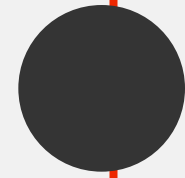

Supan Roy
ID: 232-15-716

Negative Feedback Basics

Negative feedback occurs when the feedback energy (voltage or current) opposes the input signal. This happens because the feedback signal is out of phase with the input signal.

How it Works:

- The amplifier creates a phase shift of 180° in the circuit.
- The feedback network is designed with no additional phase shift (0°), so the feedback signal is 180° out of phase with the input, effectively reducing the input signal.

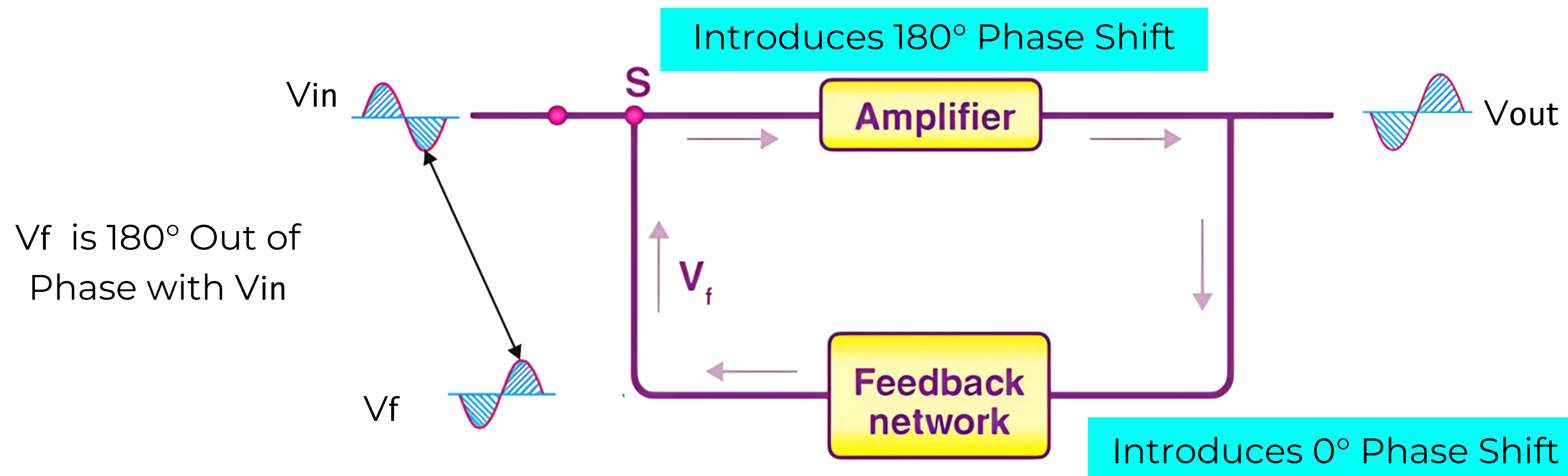


Fig. 1

Principles of Negative Voltage Feedback

In a negative voltage feedback amplifier, a portion of the output (e.g., 100 mV from a 10 V output) is fed back to the input through a feedback circuit, typically made of resistors. When combined with the input signal (101 mV), the effective input becomes 1 mV due to the negative feedback. This stabilizes the amplifier by reducing fluctuations at the input.

Referring to Fig. 2, we have,

Gain of amplifier without feedback,

$$A_v = \frac{10 \text{ V}}{1 \text{ mV}} = 10,000$$

Fraction of output voltage feedback, $m_v = \frac{100 \text{ mV}}{10 \text{ V}} = 0.01$

Gain of amplifier with negative feedback, $A_{vf} = \frac{10 \text{ V}}{101 \text{ mV}} = 100$


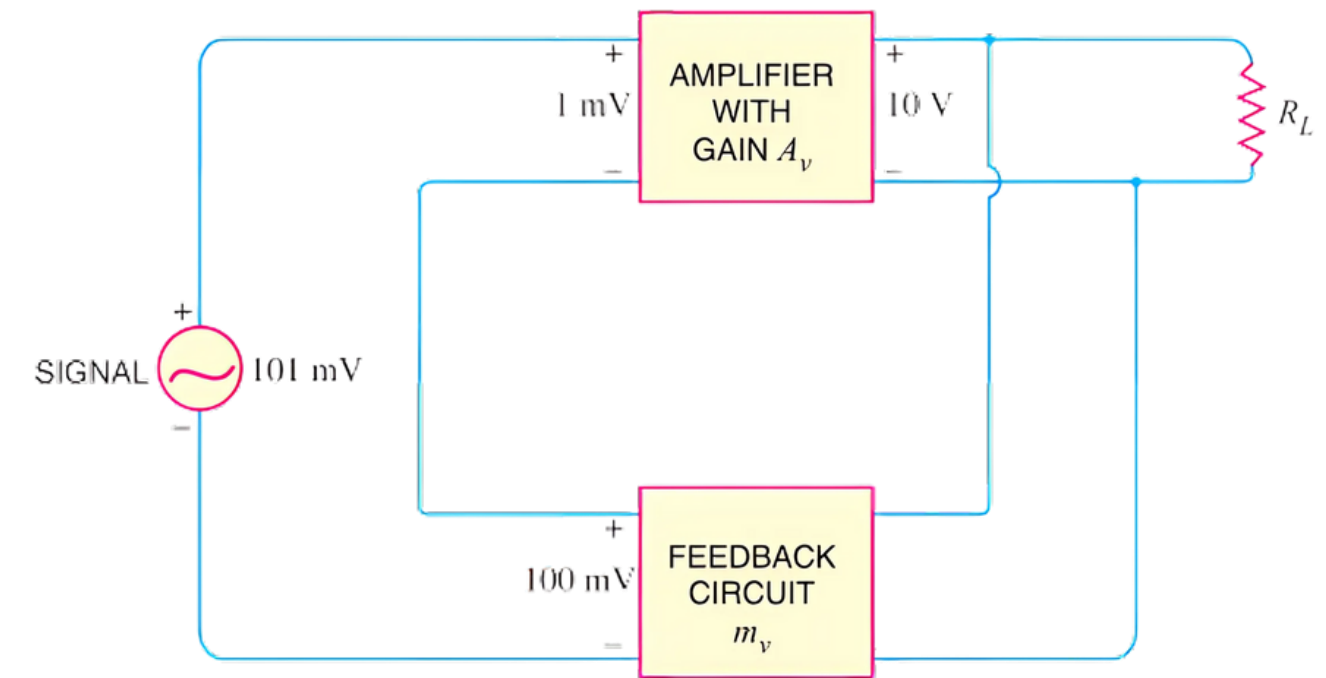


Fig. 2

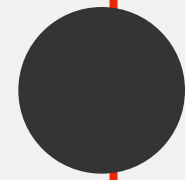

Presenter 3



Foysal Mahamud Fahim
ID: 232-15-334

Gain of Negative Voltage Feedback Amplifier

Considering the negative voltage feedback amplifier shown in the Fig. The gain of the amplifier without feedback is A_v . Negative feedback is then applied by feeding a fraction m_v of the output voltage e_o back to amplifier input. Therefore, the actual input to the amplifier is the signal voltage e_g minus feedback voltage $m_v e_o$

Actual input to amplifier = $e_g - m_v e_o$

The output e_o must be equal to the input voltage $e_g - m_v e_o$ multiplied by gain A_v of the amplifier -

$$\begin{aligned} (e_g - m_v e_o) A_v &= e_o \\ \text{or, } A_v e_g - A_v m_v e_o &= e_o \\ \text{or, } e_o (1 + A_v m_v) &= A_v e_g \\ \text{or, } \frac{e_o}{e_g} &= \frac{A_v}{1 + A_v m_v} \end{aligned}$$

But e_o/e_g is the voltage gain of the amplifier with feedback.

\therefore Voltage gain with negative feedback is

$$A_{vf} = \frac{A_v}{1 + A_v m_v}$$


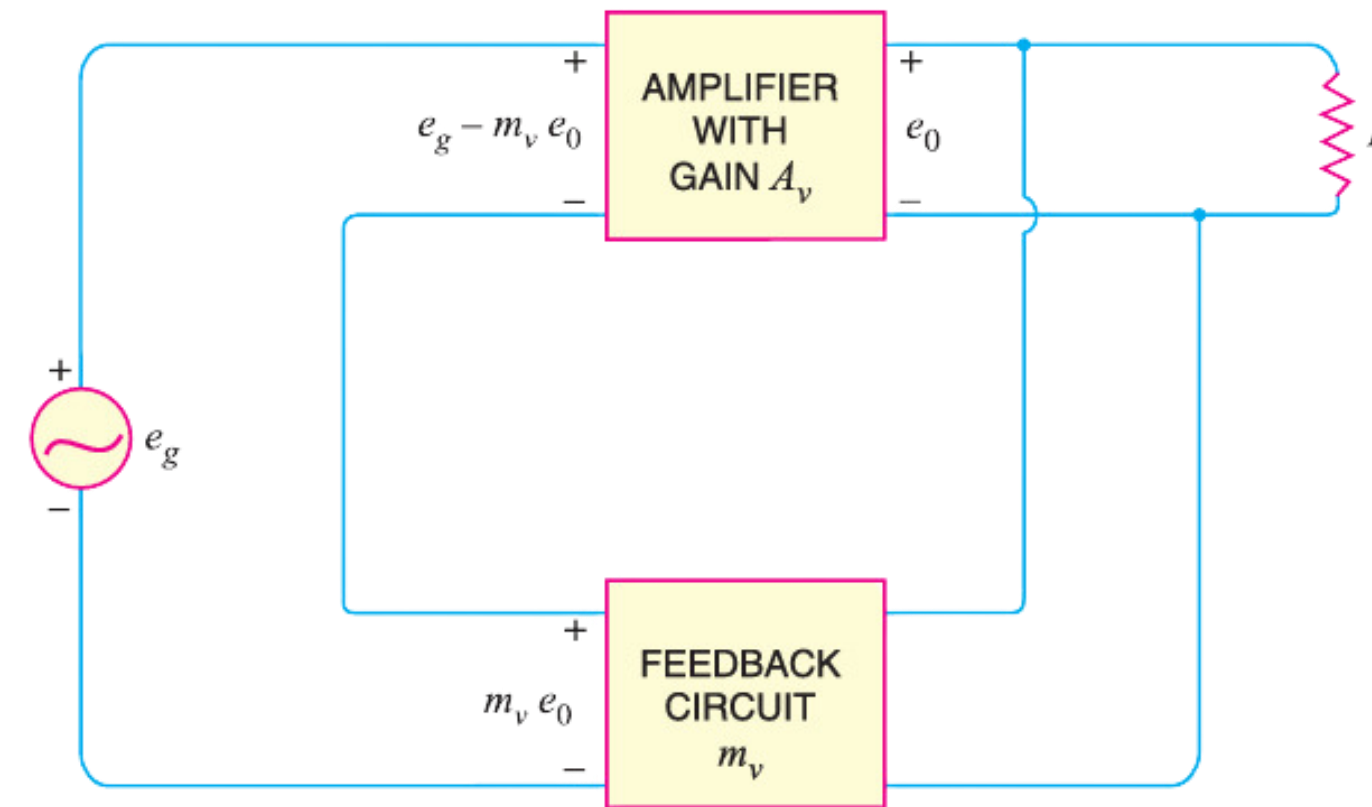


Fig. 5

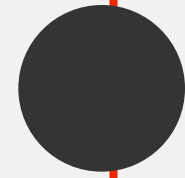

Presenter 4



Sharmin Akter Jame
ID: 232-15-380


Positive Feedback Basics

Positive feedback occurs when the feedback energy (voltage or current) is in phase with the input signal, reinforcing it rather than opposing it.

This in-phase feedback increases the amplifier's overall gain.

How it Works:

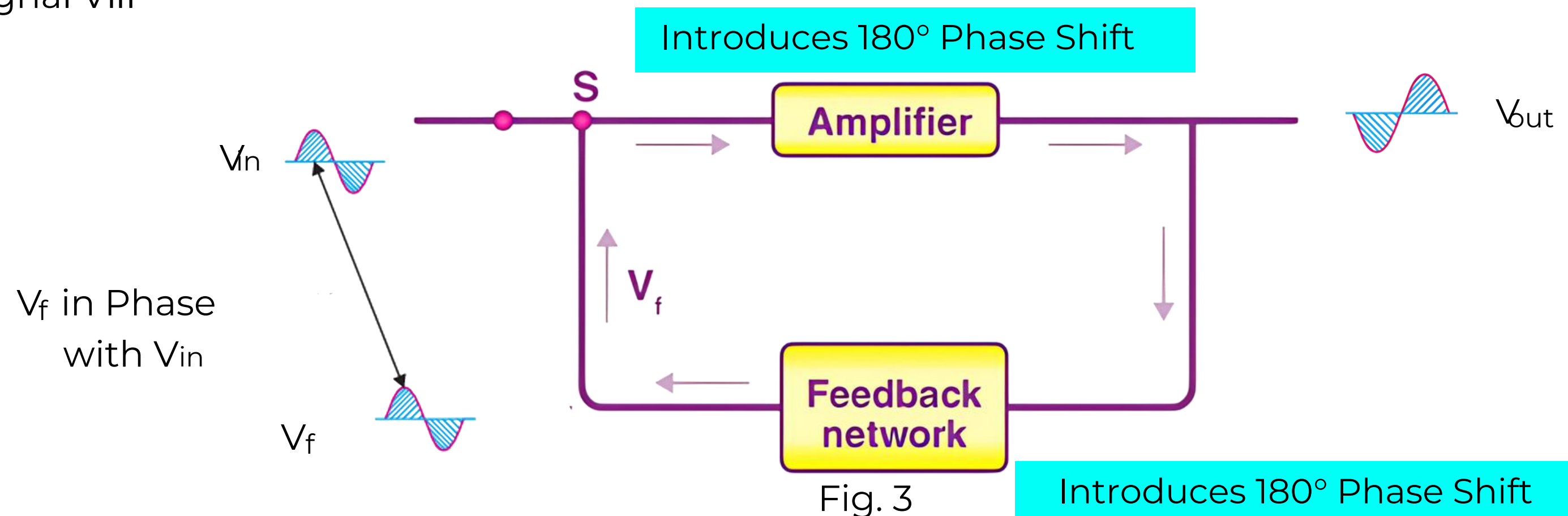- When the feedback energy (voltage or current) is in phase with the input signal and thus aids it, it is called positive feedback. Both amplifier and feedback network introduce a phase shift of 180° . The result is a 360° phase shift around the loop, causing the feedback voltage V_f to be in phase with the input signal V_{in} .



Gain of Positive Voltage Feedback Amplifier

In a positive voltage feedback amplifier, a fraction (m_v) of the output (e_o) is fed back to the input, adding to the input signal (e_g). This reinforces the input, increasing the overall gain of the amplifier.

Actual input to amplifier = $e_g + m_v e_o$

The output e_o must be equal to the input voltage $e_g + m_v e_o$ multiplied by gain A_v of the amplifier -

$$\begin{aligned}(e_g + m_v e_o) A_v &= e_o \\ \text{or, } A_v e_g + A_v m_v e_o &= e_o \\ \text{or, } e_o (1 - A_v m_v) &= A_v e_g \\ \text{or, } \frac{e_o}{e_g} &= \frac{A_v}{1 - A_v m_v}\end{aligned}$$

But e_o/e_g is the voltage gain of the amplifier with feedback.

\therefore Voltage gain with negative feedback is

$$A_{vf} = \frac{A_v}{1 - A_v m_v}$$


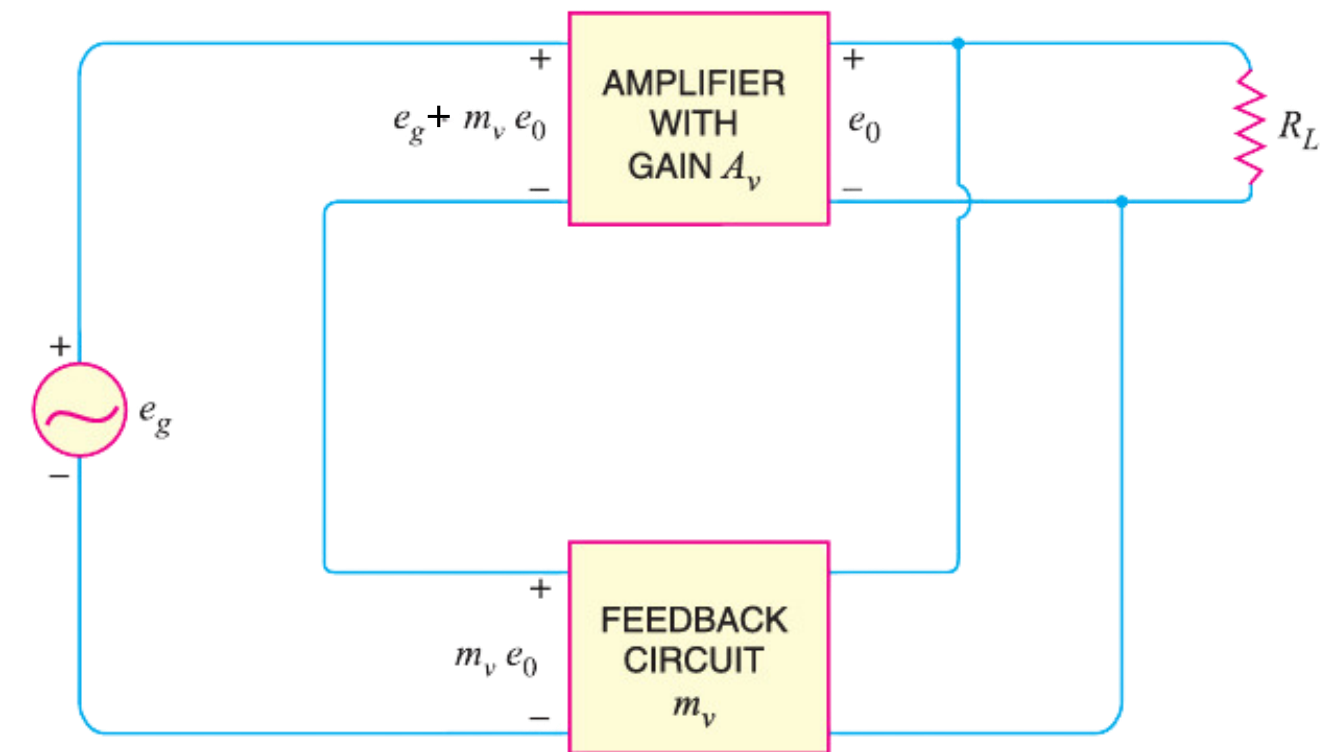


Fig. 4

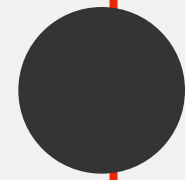

Presenter 5



Md Shahinur Kabir Antor
ID: 232-15-159

Mathematical Problems

Example 1. The overall gain of a multistage amplifier is 140. When negative voltage feedback is applied, the gain is reduced to 17.5. Find the fraction of the output that is feedback to the input.

Solution.

$$A_v = 140, \quad A_{vf} = 17.5$$

Let m_v be the feedback fraction. Voltage gain with negative feedback is

$$A_{vf} = \frac{A_v}{1 + A_v m_v}$$

or
$$17.5 = \frac{140}{1 + 140 m_v}$$

or
$$17.5 + 2450 m_v = 140$$

$\therefore m_v = \frac{140 - 17.5}{2450} = \frac{1}{20}$

Mathematical Problems

Example 2. An amplifier has a voltage gain of 500 without feedback. If a negative feedback is applied, the gain is reduced to 100. Calculate the fraction of the output fed back. If, due to ageing of components, the gain without feedback falls by 20%, calculate the percentage fall in gain with feedback.

Solution.

$$A_v = 500 ; A_{vf} = 100 ; m_v = ?$$

$$A_{vf} = \frac{A_v}{1 + A_v m_v}$$

or

$$100 = \frac{500}{1 + 500 m_v}$$

\therefore

$$m_v = 0.008$$

Now

$$A_v = \frac{80}{100} \times 500 = 400 ; m_v = 0.008 ; A_{vf} = ?$$


$$A_{vf} = \frac{A_v}{1 + A_v m_v} = \frac{400}{1 + 400 \times 0.008} = \frac{400}{4.2} = 95.3$$

\therefore

$$\% \text{ age fall in } A_{vf} = \frac{100 - 95.3}{100} \times 100 = 4.7\%$$



Presenter 6

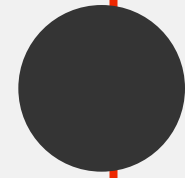


Pallab Debnath
ID: 232-15-676

Advantages of Negative Feedback in Amplifiers

- 1. Gain Stability:** Maintains a stable gain despite variations in transistor parameters or supply voltage.
- 2.Reduces Non-Linear Distortion:** Decreases distortion in large-signal amplifiers by a factor of $1 + A_{vmv}$.
- 3.Improves Frequency Response:** Keeps voltage gain steady across a range of frequencies, enhancing frequency response.
- 4.Increases Circuit Stability:** Stabilizes output against changes in temperature, frequency, and amplitude.
- 5.Increases Input Impedance & Decreases Output Impedance:** Facilitates impedance matching, benefiting practical applications.



Presenter 7

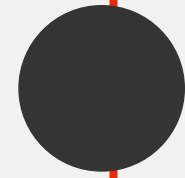

Umme Arifa Zaman Nirjhor
ID: 232-15-695

Comparison between Positive and Negative Feedback

Aspect	Negative Feedback	Positive Feedback
Phase Relationship	Feedback signal is out of phase with the input signal (opposes it).	Feedback signal is in phase with the input signal (reinforces it).
Effect on Gain	Reduces overall gain but increases stability and accuracy.	Increases gain and can lead to oscillations if uncontrolled.
Stability	Improves stability and reduces sensitivity to component changes.	Can reduce stability, often leading to oscillations; useful in oscillators.
Distortion and Noise	Reduces distortion and filters noise; ideal for high-fidelity applications.	Can increase distortion; not typically used where clean signal output is critical.
Typical Applications	Used in audio amplifiers, control systems, and op-amp circuits for stable gain.	Applied in oscillators, Schmitt triggers, and RF amplifiers for signal generation.

Conclusion

Feedback Types:

- **Negative Feedback:** Reduces gain, stabilizes performance, and lowers distortion.
- **Positive Feedback:** Increases gain, used for oscillations and signal shaping.

Key Points:

- **Negative Feedback:** Ideal for stable, high-quality output.
- **Positive Feedback:** Useful in circuits needing oscillation, like oscillators and triggers.

Real-World Impact:

- Feedback amplifiers are essential in audio, communications, and control systems.



Thank You

