

SUPER SENSITIVE INTRUDER ALARM

P R O J E C T P R E S E N T A T I O N

Presented to –

Mr. Shoumik Debnath

Lecturer,

Department of CSE

Daffodil International University



GROUP 4

65_D1

OUR TEAM

SUPAN ROY
ID: 232-15-716

ABDULLAH AL NOMAN
ID: 232-15-797

NUR SAYDA
ID: 232-15-437

MD. SHAHINUR KABIR ANTOR
ID: 232-15-159

SHAKIRA RAHMAN SIMI
ID: 232-15-723



Introduction

- ◆ *In today's world, security is a major concern for homes, offices, and restricted areas.*
- ◆ *Our project focuses on building a cost-effective and highly sensitive **intruder alarm system** using basic electronic components.*
- ◆ *The system uses **infrared (IR)** technology to detect motion or interruption in the IR beam.*
- ◆ *When someone blocks it, the alarm turns on, the system triggers a **buzzer** to alert about the intrusion.*
- ◆ *This kind of setup can help improve **safety and awareness** in any environment.*
- ◆ *This project is ideal for beginners and can be expanded for real-life security applications.*





COMPONENTS USED

1. *NE555 Timer IC*
2. *LM358 Operational Amplifier (Op-Amp)*
3. *10K Preset/Variable resistor*
4. *IR Transmitter*
5. *IR Receiver*
6. *Red LED*
7. *Electrolytic Capacitor (10uF, 50V)*
8. *Resistors: 10K Ω , 1K Ω , 100K Ω , 220 Ω*
9. *Buzzer*
10. *Breadboard*
11. *Connecting Wires Multiple*
12. *5V Power Supply*



Circuit Diagram

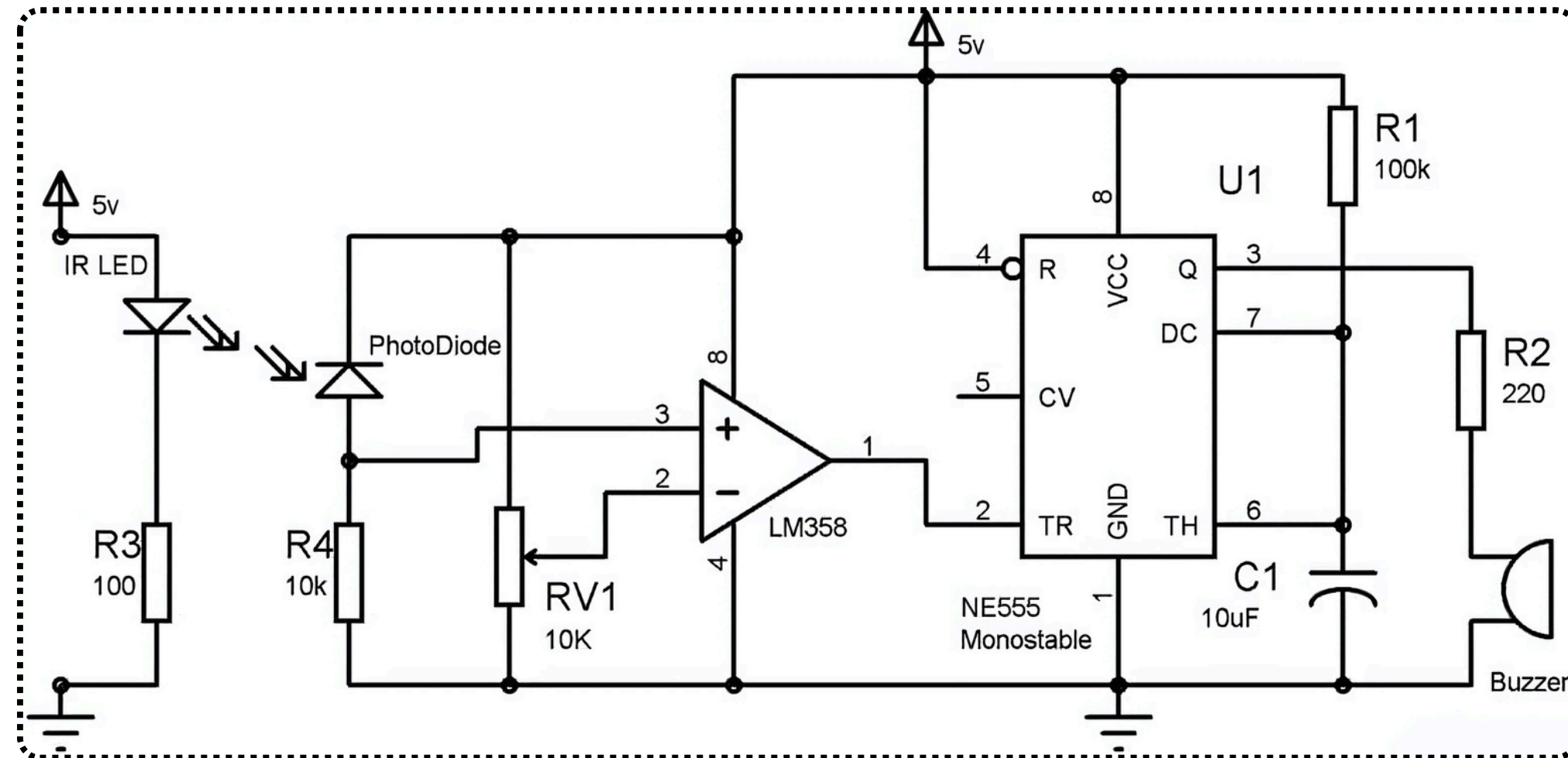


Fig. 1.1: Super Sensitive Intruder Alarm Circuit

Project Prototype

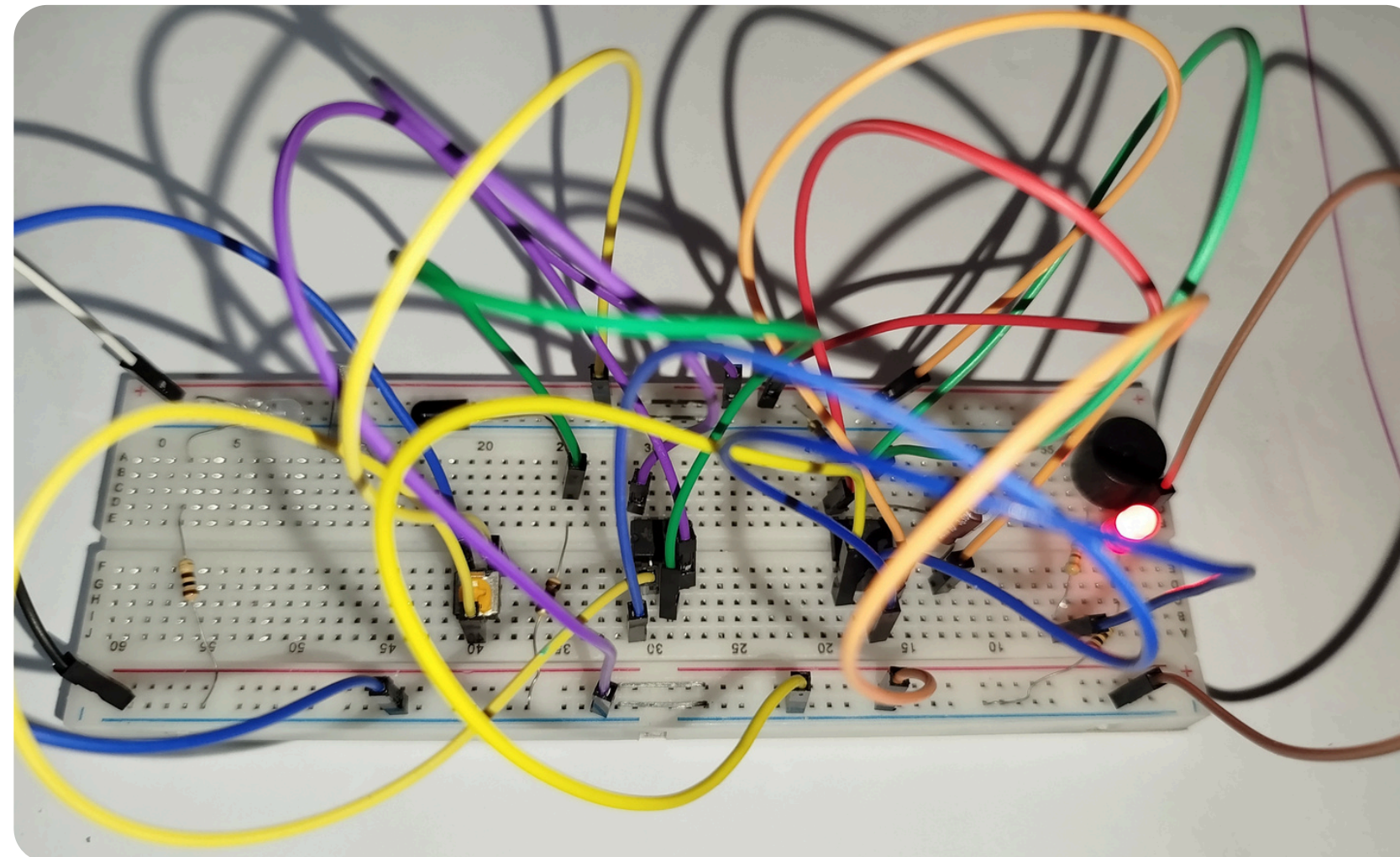


Fig. 1.2: Super Sensitive Intruder Alarm Circuit

WORKING PRINCIPLE

⚙️ 1. IR Transmitter Section

- *IR LED emits invisible infrared light continuously.*
- *100Ω Resistor (R3) limits current to protect the IR LED.*
- *Light beam is aimed at the photodiode across the sensing area.*

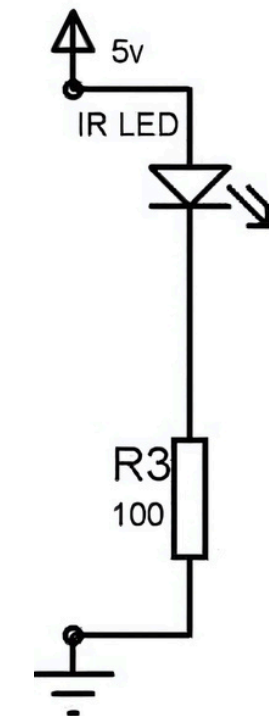


Fig. 2.1: IR Transmitter



WORKING PRINCIPLE

👁 2. IR Receiver & Comparator Section

- Photodiode is in reverse bias: receives IR light and allows reverse current.
- **10k Ω** Resistor (R4) works as a pull-down resistor, creating a voltage drop based on IR light intensity.
- **10k Ω** Preset (RV1) sets a fixed reference voltage at **LM358**'s inverting input.

LM358 Op-Amp (Comparator) compares:

- Pin 3 (+): voltage from photodiode
- Pin 2 (-): reference from preset

When someone blocks IR beam:

- Photodiode voltage increases (Pin 3 > Pin 2)
- Comparator output (Pin 1) goes LOW to HIGH, triggering next stage

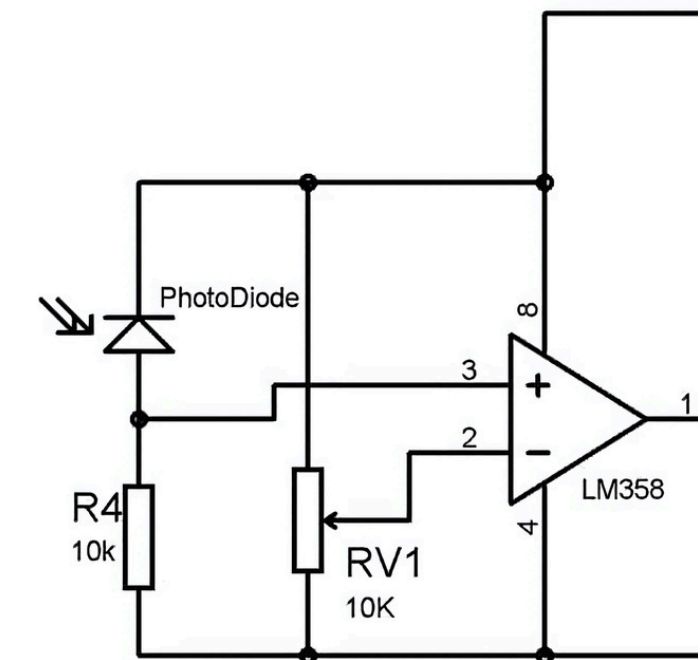


Fig. 2.2: IR Receiver and Op-Amp (LM358)



WORKING PRINCIPLE

🕒 3. Monostable Timer Section (555 IC)

- **NE555** Timer is configured in monostable mode.
- Trigger Pin (Pin 2) is activated by **LM358** output.
- **100kΩ** Resistor (R1) and 10μF Capacitor (C1) define the ON-time.

On trigger:

- Pin 3 (Output) goes HIGH for a fixed duration.
- Timer resets automatically after time interval ends.

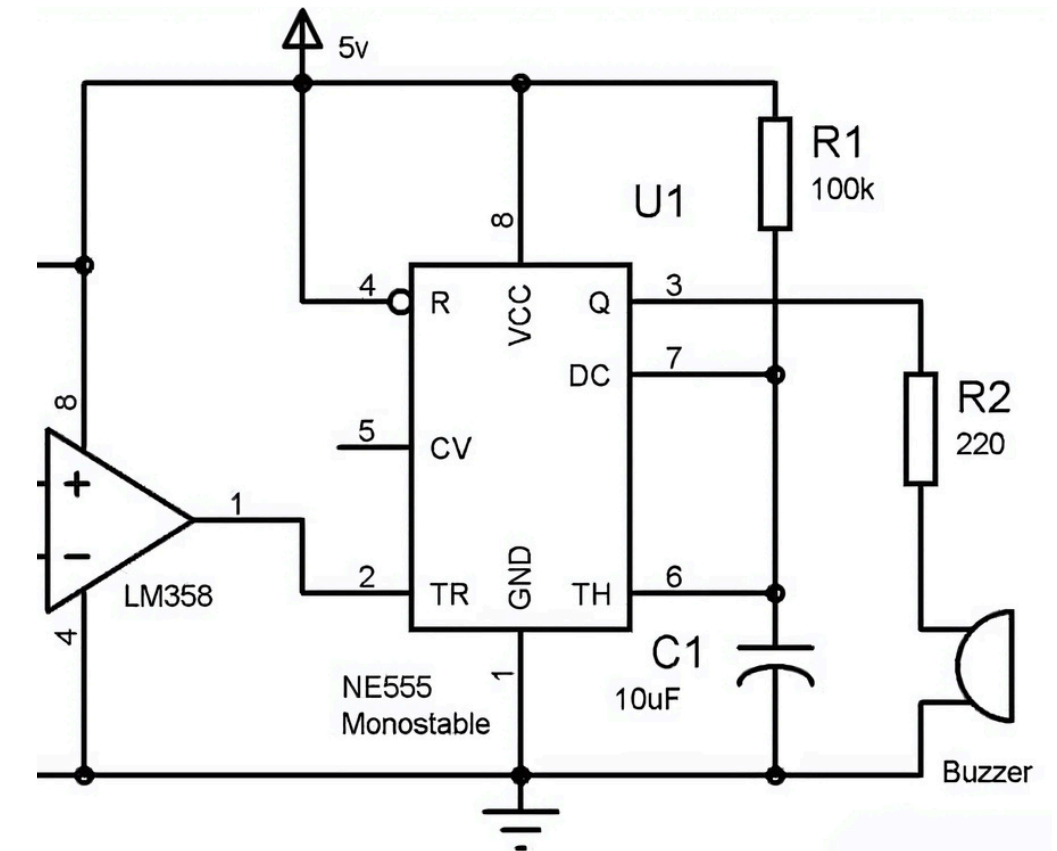



Fig. 2.3: 555 Timer IC



WORKING PRINCIPLE

🔔 4. Output Section (Buzzer)

- **220Ω** Resistor (R2) limits current to the Buzzer.
- When 555 output is HIGH:
 - Buzzer turns ON
 - Produces alert sound indicating intrusion
-  **Power Supply:**
 - Whole circuit operates on **+5V DC** supply.
 - All ICs and components are powered from this single source.

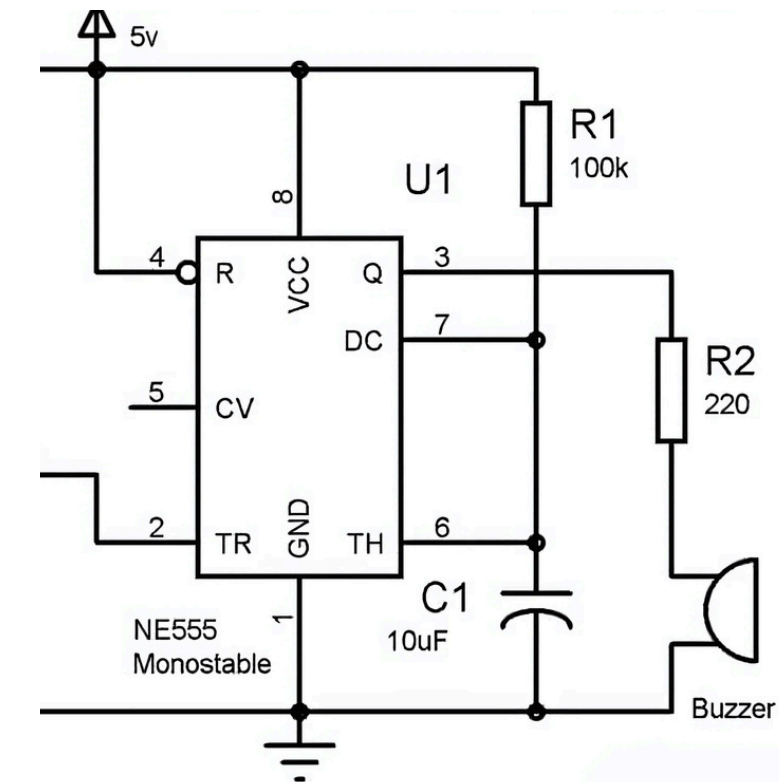


Fig. 2.4: Buzzer Output





Applications & Future Improvements

APPLICATIONS:

◆ **Home Security Systems**

Used at doors, windows, or hallways to detect unauthorized entry.

◆ **Bank & ATM Booths**

Alerts security when someone enters during off-hours.

◆ **Warehouses & Storage Units**

Protects valuable goods from theft by detecting movement.

◆ **School Labs or Server Rooms**

Restricts access to sensitive areas when unsupervised.

◆ **Automatic Lighting Systems**

Can be adapted to turn on lights when someone enters a room.





Applications & *Future Improvements*



FUTURE IMPROVEMENTS:

- ◆ Add **SMS** or **Call Alert** feature using GSM module.
- ◆ Integrate with **CCTV systems** for real-time footage during intrusion.
- ◆ Make it **battery powered** for portability and use during power cuts.
- ◆ Add **Wi-Fi or IoT** support to control and monitor via smartphone.
- ◆ Use motion sensors or **camera-based** detection for more accuracy.





Learning Outcomes



◆ Understanding Real-world Problem Solving

We learned how basic electronics can be applied to real-life security issues in a cost-effective way.

◆ Circuit Design & Implementation

We gained hands-on experience building a working circuit using sensors, op-amps, and timers.

◆ Sensor Technology

Understood how IR sensors work and how they can be used to detect objects or people non-contact.

◆ Comparator and Timer Logic

Learned how a comparator (LM358) compares voltages and how a 555 timer functions in monostable mode.

◆ Troubleshooting & Debugging

Faced practical issues like incorrect wiring, loose connections, and fixed them to make the circuit stable.





CONCLUSION

In this project, we successfully designed and implemented a **Super Sensitive Intruder Alarm** that can detect **unauthorized entry** using an infrared sensor system. The circuit provides a quick and reliable alert whenever the **IR beam** is interrupted, making it a practical solution for basic security needs. Through this work, we not only built a **functional security system** but also gained valuable knowledge about **sensor technology**, **circuit design**, and **component integration**. This project helped strengthen our teamwork and problem-solving abilities, and with future improvements, the system holds potential for real-world applications in homes, schools, and other secure areas.



THANK YOU!

F O R Y O U R A T T E N T I O N

